

Kevin Gomes
Dr. Baudet
CSC 411
21 November 2017
Assignment #7

Reference point:

F1	F0	Operation
0	0	X OR Y = Z
0	1	X AND Y = Z
1	0	NOT Y = Z
1	1	X XOR Y = Z

Memory Addresses:

X1	X0	Address points to...
0	0	A
0	1	B
1	0	C
1	1	D

Order of instruction:

F1F0 X1X0 Y1Y0 Z1Z0

NOTE: All comments will be denoted by a **semi-colon ;** at the start of the line. If we use a block comment, we will use a square bracket to denote the start after the semi-colon, and end it with a square bracket followed by semi-colon. The last comment will contain the complete code to make it easier to read. The following are examples of how I will comment.

;[this

Is a block comment.

Still in the comment!


];

;This is a regular comment. It is outside of the block comment.

; Another regular comment.

Step 1: Implement, using basic 2-input gates, a 3-bit majority function.

 NOTE: I realize we could instead make it simply $AB + (A \text{ XOR } B) \text{ AND } C$. But I wanted to use basic logic gates for this one. I've grown fond of them :)



Step 2: Implement that same 3-bit majority function using binary operations with the Puny Computer. Comment it. Can destroy contents of any register.

```
00 01 10 11
```

```
:[^B + C = D    This makes register D store the value of B OR C, which is that first OR gate in the logic gate solution.
```

```
];
```

```
01 01 10 01
```

```
:[^BC = B       This stores the result of B AND C into register B, which is the first AND gate in the logic gate solution (bottom one)
```

```
];
```

```
01 00 11 10
```

```
:[^AD = C       This stores the result of A AND D into register C. Note that D is = B OR C (original value of B), so by substituting D with B OR C, we get A AND (B OR C). This is the top AND gate in the logic gate solution.
```

```
];
```

```
00 10 01 11
```

```
:[^C + B = D     Finally, with our registers holding the result of gates, use those results together with an OR gate. If we look above, B is = to the original values of B AND C, and C is = to the
```

original values of A AND D (which is actually A AND (B OR C)). Therefore, with substitution again, C is actually A AND (B OR C), and B is actually B AND C. Knowing this, D is equal to (A AND (B OR C)) OR (B AND C). This is reflected in our logic gate solution. Alone, the program looks as follows:

```
00 01 10 11
```


```
01 01 10 01
```

```
01 00 11 10
```

```
00 10 01 11
```

```
];
```

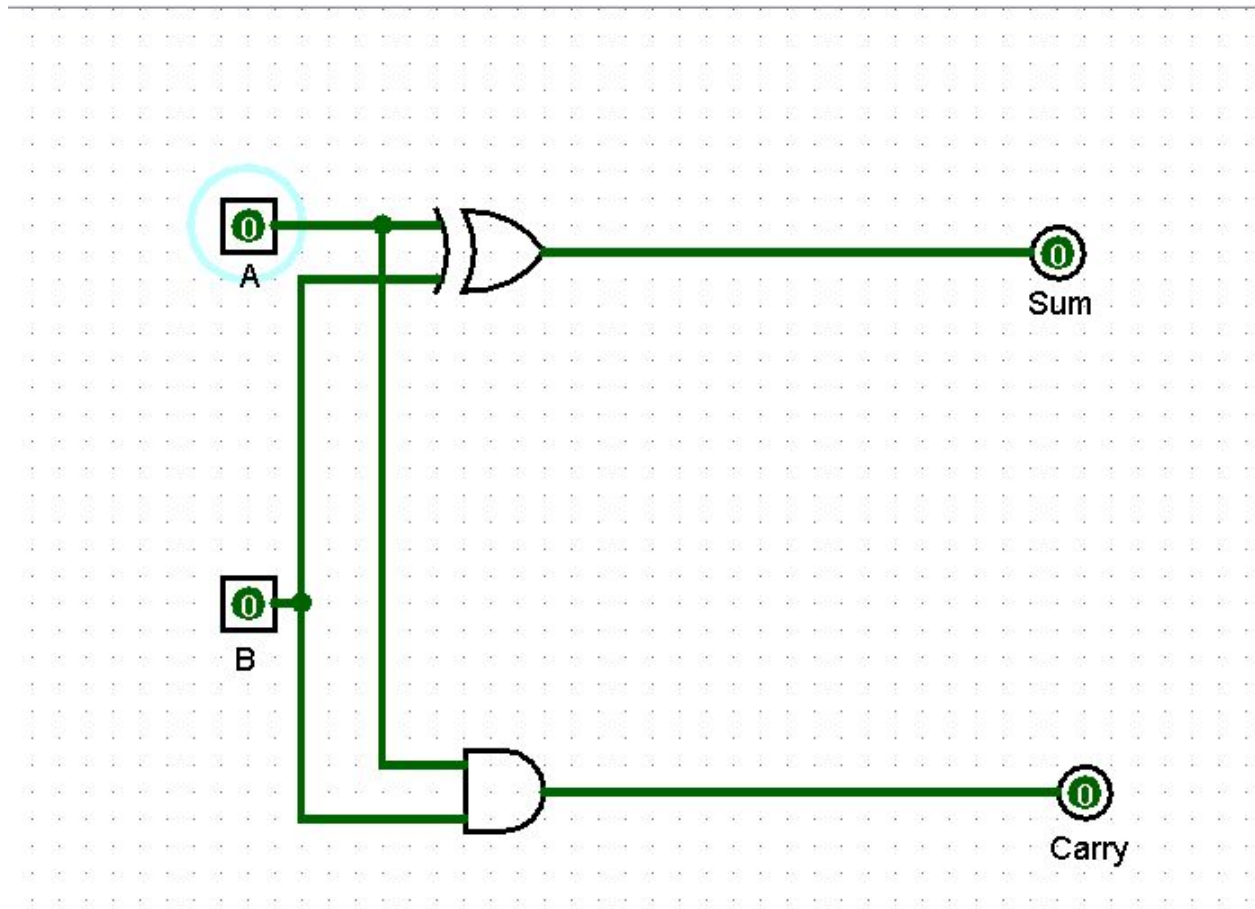Step 3: Write Half-Adder with Puny Computer. Comment it. Can destroy contents of A and B.
;[First, we will make it in logic gates so it is easier to create in Puny Computer. This practice is actually JUST like creating higher-level code, then converting it to low-level MicMac assembly code. Interesting **coincidence**.....



Now to actually make the Puny Computer code, which seems very simple...

```
];
```

```
11 00 01 11
```

[;^ A XOR B = D Store the result of A XOR B (the inputs) into register D. This is the sum.
Not much to say here.

];

01 00 01 10

[;^ AB = C Store the result of A AND B into register C, which is the carry. Because $1 + 1 = 2$,
but we only have 1 and 0, we must carry a 1 to the next spot, which is used in the full adder.

Our final program, in pretty form:


11 00 01 11

01 00 01 10

];

Step 4: Write Full-Adder with Puny Computer. Comment it. Can change contents of original C, A and B.

[; Obviously, the Full-Adder uses Half-Adders in its implementation, so when we make the logic gates, we will use the module Half-Adder not as a box, but with its implementation taken out. This is to make it easier to see what's going on. Note that due to having 4 registers, we will simply change what C is to replicate the output C (it is at first whatever the input is, but we change it to be what it should be).

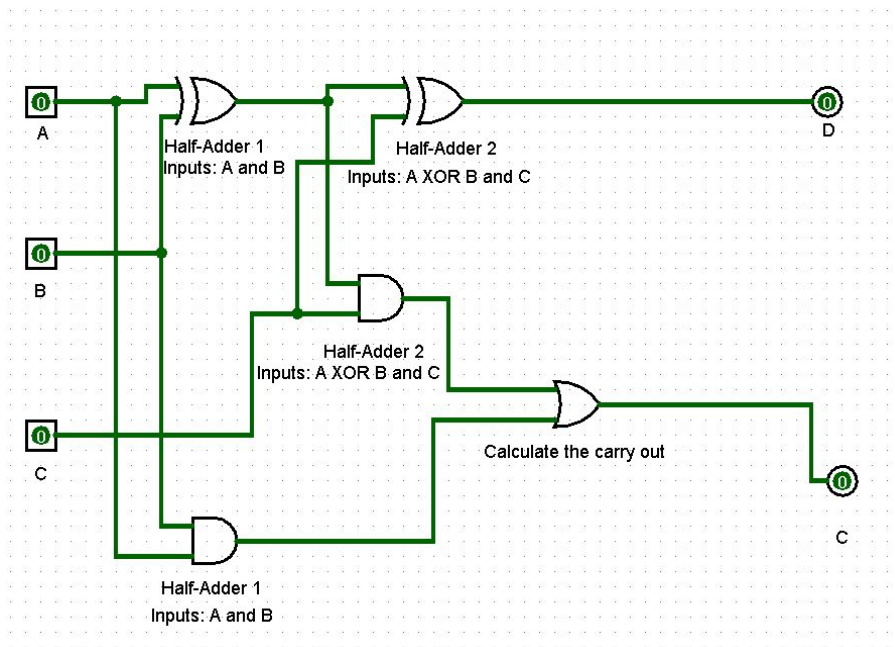

Now to code it.];

11 00 01 11

[;^ A XOR B = D so now D (which eventually will be sum) has contents of first XOR (A XOR B)];

01 00 01 01

[;^ AB = B So B has the contents of A AND B, which is the 1st AND from the left (the original value of B is used here, and now B has a new value). Note that in doing this, we now realize we no longer need the original values of A and B. We used A for both of its uses (A XOR B and A AND B), and B for both of its uses (the same uses). By doing this, A is now a freed register with which we can use in any way, and B is now A AND B (original value of A)];

00 11 11 00

[;^ D + D = A For organization, we put the value of D into A. It is impossible to simply say $X = Y$, so we say $X \text{ OR } X = Y$ because $X \text{ OR } X$ just reduces to X . Now we have A being A XOR B, and B being A AND B];

11 00 10 11

[;^ A XOR C = D Basically, this forms as (A XOR B) XOR C = D. Remember before we set A to be the previous value of D, which was A XOR B. This is the final sum (the 2nd XOR from the left)! We are done with the sum.];

01 00 10 10

[;^ AC = C So now we have (A XOR B) AND C, which is that AND in the middle of the diagram, 2nd from the left. We changed the carry-in to be this, because just like the case of A and B, we no longer need the original value for any operations, as we already used it for the sum!];

00 01 10 10

[;^ B + C = C With B being A AND B, and C being (A XOR B) AND C, we now test for if either is true. This basically means if A and B are 1, or one of them is 1 AND C is 1, then make that the carry out. It's basically a better majority function than mine in step 1, as any 2 that are on results in a 1. After this, the carry-out and sum (C and D, respectively) are set, and we are finished

Our final code, in pretty form:

11 00 01 11

01 00 01 01

00 11 11 00

11 00 10 11

01 00 10 10

00 01 10 10

];